

深圳大学实验报告

课程名称： 硬件描述语言及数字系统设计

实验项目名称： 实验三 七段数码管显示

学院： 医学院

专业： 生物医学工程

指导教师： 但果、董磊

报告人： 陈焕鑫 学号： 2016222042 班级： 生工 2 班

实验时间： 2018.10.24

实验报告提交时间： 2018.11.2

教务部制

一、实验平台：

安装了 ISE 软件的 PC 计算机
硬件描述语言及数字系统设计实验平台
JTAG 下载线

二、实验目的：

当你完成整个项目之后，你将会学会一下内容：

- 掌握七段数码管显示原理
- 能够用拨位开关控制数码管的显示

三、实验内容：

- 用 VHDL 代码描述一个七段数码管的译码电路，并编写测试激励进行测试
- 编写引脚约束文件，用 ISE 软件生产 .bit 文件，下载到硬件描述语言及数字系统设计实验平台进行板级验证

四、实验原理：

七段数码管实际上是由八个发光二极管（a, b, c, d, e, f, g, dp）组成，如图 4-1 所示，每个发光二极管对应数码管中的一段，不同发光二极管的组合形成不同的字符。如发光二极管除了 dp 段以外都发光，显示出来的字符就是“8”，b, c 两个二极管发光则形成“1”等。

 


图 4-1

为了使发光二极管正确发光，需要有“七段数码管译码器”，“七段数码管译码器”的作用是把 0-F 字符的二进制信号转变成七个发光二极管的发光信号。

“七段数码管译码器”由四个输入端来控制，七个输出端 a, b, c, d, e, f, g 输出二极管的发光信号（小数点暂时不用）。

七段数码管分为共阳型和共阴型，如图 4-2 所示。硬件描述语言及数字系统设计实验平台上的七段数码管属于共阳型，因此译码输出为“1”表示发光二极管熄灭，译码输出为“0”则表示发光二极管点亮。七段数码管的各段按照从高位到低位的顺序依次是 dp g g e d c b a，例如，参照图 4-1，就可以得出“0”字符的译码结果为 11000000。用 4 位二进制数字表示 0-F，那么就可以得出七段数码管的译码表如表 4-1 所示

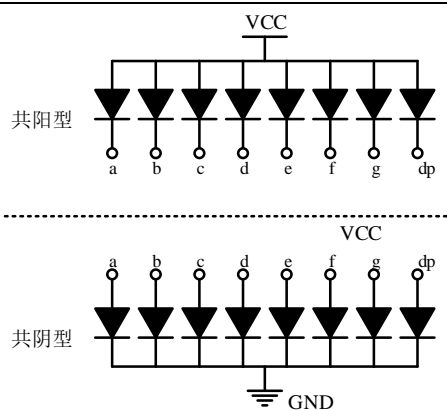


图 4-2

| 四位输入 | 八位输出 (dp g f e d c b a) | 显示字符 |
|------|-------------------------|------|
| 0000 | 11000000 (0xC0) | 0 |
| 0001 | 11111001 (0xF9) | 1 |
| 0010 | 10100100 (0xA4) | 2 |
| 0011 | 10110000 (0xB0) | 3 |
| 0100 | 10011001 (0x99) | 4 |
| 0101 | 10010010 (0x92) | 5 |
| 0110 | 10000010 (0x82) | 6 |
| 0111 | 11111000 (0xF8) | 7 |
| 1000 | 10000000 (0x80) | 8 |
| 1001 | 10010000 (0x90) | 9 |
| 1010 | 10001000 (0x88) | A |
| 1011 | 10000011 (0x83) | b |
| 1100 | 11000110 (0xC6) | C |
| 1101 | 10100001 (0xA1) | d |
| 1110 | 10000110 (0x86) | E |
| 1111 | 10001110 (0x8E) | F |

表 4-1 七段数码管译码表

五、实验方法步骤及 VHDL 代码：

根据分频原理进行代码设计，设计一个产生 1Hz 的时钟信号。

具体的 VHDL 代码如下所示：

```
-----  
--模块名称: clk_gen_1hz  
--摘要提示:  
--当前版本: 1.0.0  
--模块作者:  
--完成日期: 20xx 年 xx 月 xx 日  
--内容提要:  
--需要注意:  
-----  
  
--取代版本:  
--模块作者:  
--完成日期:  
--修改内容:  
--修改文件:  
-----  
  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
  
-----ENTITY DECLARATION-----  
entity clk_gen_1hz is  
    generic(  
        CNT_MAX : integer := 50000000; --计数的最大值  
        CNT_HALF: integer := 25000000  --计数最大值的一半  
    );  
  
    port(  
        rst_n_i : in  std_logic;      --复位信号输入端口  
        clk_i   : in  std_logic;      --时钟信号输入端口  
        clk_o   : out std_logic       --时钟信号输出端口  
    );  
end clk_gen_1hz;  
  
-----ARCHITECTURE STRUCTURAL-----  
architecture rtl of clk_gen_1hz is  
  
    signal s_cnt : integer range 0 to CNT_MAX := 0;
```

```

begin

process(clk_i, rst_n_i, s_cnt)
begin
    if(rst_n_i = '0')then    --复位信号优先级别较高
        s_cnt <= 0;
        clk_o <= '0';
    elsif rising_edge(clk_i) then --每来一个时钟信号上升沿
        if (s_cnt = CNT_MAX) then    --计数到最大值
            s_cnt <= 0;                --重新开始计数
            clk_o <= '0';            --时钟输出信号拉低
        elsif (s_cnt = CNT_HALF) then --计数到一半时
            s_cnt <= s_cnt + 1;        --计数值加 1
            clk_o <= '1';            --时钟信号输出拉高
        else
            s_cnt <= s_cnt + 1;        --计数值加 1
        end if;
    end if;
end process;

end rtl;

```

秒钟计数器模块-sec_counter，每接收到一次 1Hz 的上升沿信号，秒钟计数器就加 1，直到计数达到 59 时，再接收到 1Hz 信号计数器将清零，同时分钟进位端输出“1”

--模块名称: sec_counter

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

use IEEE.STD_LOGIC_ARITH.ALL;

```

```

use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity sec_counter is
    Port (
        clk_i : in  STD_LOGIC;           --时钟信号输入端
        rst_n_i : in  STD_LOGIC;         --复位信号输入端
        sec_cnt_o : out STD_LOGIC_VECTOR (5 downto 0); --秒数输出端
        min_carry_o : out STD_LOGIC      --分钟进位端
    );
end sec_counter;

architecture rtl of sec_counter is
    signal s_carry : std_logic := '0';
    signal s_sec   : std_logic_vector(5 downto 0) := "000000";

begin
    process(clk_i, rst_n_i)
    begin
        if(rst_n_i = '0')then --如果复位信号有效
            s_carry <= '0';      --进位端输出 0
            s_sec   <= "000000"; --秒数端输出 0
        elsif rising_edge(clk_i)then --时钟上升沿
            if(s_sec = "111011")then --如果大于 59
                s_sec <= "000000";
                s_carry <= '1';
            else
                s_sec <= s_sec + "000001";
                s_carry <= '0';
            end if;
        end if;
    end process;
    sec_cnt_o <= s_sec;
    min_carry_o <= s_carry;
end rtl;

```

分钟计数器模块-min_counter，每接收到一次分钟进位输出的上升沿信号，分钟计数器就加 1，直到计数达到 59 时，再接收到分钟进位信号计数器将清零，同时时钟进位端输出“1”

--模块名称: min_counter

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

```

--需要注意:
-----

--取代版本:
--模块作者:
--完成日期:
--修改内容:
--修改文件:
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity min_counter is
    Port (
        clk_i : in STD_LOGIC; --时钟信号输入端
        rst_n_i : in STD_LOGIC; --复位信号输入端
        min_cnt_o : out STD_LOGIC_VECTOR (5 downto 0); --分钟输出端
        hour_carry_o : out STD_LOGIC --时钟进位端
    );
end min_counter;

architecture rtl of min_counter is
    signal s_carry : std_logic := '0';
    signal s_min : std_logic_vector(5 downto 0) := "000000";

begin
    process(clk_i, rst_n_i)
    begin
        if(rst_n_i = '0')then --如果复位信号有效
            s_carry <= '0';
            s_min <= "000000";
        elsif rising_edge(clk_i) then --如果在时钟上升沿
            if(s_min = "111011") then --如果大于 59
                s_min <= "000000";
                s_carry <= '1';
            else
                s_min <= s_min + "000001";
                s_carry <= '0';
            end if;
        end if;
    end process;

    min_cnt_o <= s_min;
    hour_carry_o <= s_carry;
end

```

```
end rtl;
```

时钟计数器模块-hour_counter，每就收到一次时钟进位输出的上升沿信号，时钟计数器就加 1，直到计数达到 23 时，再收到时钟进位信号计数器将清零

--模块名称: hour_counter

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity hour_counter is
```

```
    Port (
```

```
        clk_i : in  STD_LOGIC;      --时钟信号输入端
```

```
        rst_n_i : in  STD_LOGIC;    --复位信号输入端
```

```
        hour_cnt_o : out STD_LOGIC_VECTOR (5 downto 0) --时钟输出端
```

```
    );
```

```
end hour_counter;
```

```
architecture rtl of hour_counter is
```

```
    signal s_hour : std_logic_vector(5 downto 0) := "000000";
```

```
begin
```

```
    process(clk_i, rst_n_i)
```

```
    begin
```

```
        if(rst_n_i = '0') then      --如果复位信号有效
```

```
            s_hour <= "000000";
```

```
        elsif rising_edge(clk_i) then --如果在时钟上升沿
```

```
            if(s_hour = "10111") then --如果大于 23
```

```
                s_hour <= "000000";
```

```
            else
```



```

        s_hour <= s_hour + "000001";
    end if;
end if;
end process;
hour_cnt_o <= s_hour;
end rtl;

```

求商模块-calc_mod，接收计数器输出的信号，转换为整型，求得除以 10 之后的商，将以 BCD 码的格式其输出

--模块名称: calc_mod

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity calc_mod is

```

```

    Port (

```

```

        data_i : in  STD_LOGIC_VECTOR (5 downto 0); --数据输入端

```

```

        data_o : out STD_LOGIC_VECTOR (4 downto 0) --数据输出端

```

```

    );

```

```

end calc_mod;

```

```

architecture rtl of calc_mod is

```

```

    signal s_data : integer range 0 to 59;

```

```

    signal s_mod  : integer range 0 to 9 ;

```

```

begin

```

```

    s_data <= conv_integer(data_i); --调用函数将 std_logic_vector 转为 Integer

```

```

    process (s_data)

```

```

begin
    if (s_data >= 0 and s_data <= 9) then
        s_mod <= 0;
    elsif (s_data >= 10 and s_data <= 19) then
        s_mod <= 1;
    elsif (s_data >= 20 and s_data <= 29) then
        s_mod <= 2;
    elsif (s_data >= 30 and s_data <= 39) then
        s_mod <= 3;
    elsif (s_data >= 40 and s_data <= 49) then
        s_mod <= 4;
    elsif (s_data >= 50 and s_data <= 59) then
        s_mod <= 5;
    end if;
end process;
data_o <= conv_std_logic_vector(s_mod,5);--再转回 std_logic_vector

end rtl;

```

求模模块-calc_rem，接收计数器输出的信号，转换为整型，求得除以 10 之后的余数，并将其以 BCD 码的格式输出

```
--模块名称: calc_rem
```

```
--摘要提示:
```

```
--当前版本: 1.0.0
```

```
--模块作者:
```

```
--完成日期: 20xx 年 xx 月 xx 日
```

```
--内容提要:
```

```
--需要注意:
```

```
--取代版本:
```

```
--模块作者:
```

```
--完成日期:
```

```
--修改内容:
```

```
--修改文件:
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity calc_rem is
```

```
    Port (
```

```

        data_i : in  STD_LOGIC_VECTOR (5 downto 0); --数据输入端
        data_o : out STD_LOGIC_VECTOR (4 downto 0) --数据输出端
    );
end calc_rem;

architecture rtl of calc_rem is
    signal s_data : integer range 0 to 59;
    signal s_rem : integer range 0 to 9;

begin
    s_data <= conv_integer(data_i); --调用函数将 std_logic_vector 转为 Integer

    process(data_i)
    begin
        if    (s_data >= 0 and s_data <= 9) then
            s_rem <= s_data;
        elsif (s_data >= 10 and s_data <= 19) then
            s_rem <= s_data - 10;
        elsif (s_data >= 20 and s_data <= 29) then
            s_rem <= s_data - 20;
        elsif (s_data >= 30 and s_data <= 39) then
            s_rem <= s_data - 30;
        elsif (s_data >= 40 and s_data <= 49) then
            s_rem <= s_data - 40;
        elsif (s_data >= 50 and s_data <= 59) then
            s_rem <= s_data - 50;
        end if;
    end process;

    data_o <= conv_std_logic_vector(s_rem,5); --再转回 std_logic_vector
end rtl;

```

因为实验箱上有 8 个数码管，为满足整个数码管在 50Hz 的闪烁频率以内，每个数码管的切换频率为 400Hz。根据分频原理进行代码设计，设计一个 400Hz 的时钟信号发生器，用于七段数码管的扫描。因为时钟晶振的频率是 50MHz，因为产生一个 400Hz 的信号需要计数 125000 次。

```

-----
--模块名称: clk_gen_400hz
--摘要提示:
--当前版本: 1.0.0
--模块作者:
--完成日期: 20xx 年 xx 月 xx 日
--内容提要:
--需要注意:
-----

```

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

entity clk_gen_400hz is
    generic(
        CNT_MAX  : integer := 125000;
        CNT_HALF : integer := 62500
    );

    Port (
        rst_n_i : in    STD_LOGIC; --复位信号输入端
        clk_i   : in    STD_LOGIC; --时钟信号输入端
        clk_o   : out   STD_LOGIC  --时钟信号输出端
    );
end clk_gen_400hz;

architecture rtl of clk_gen_400hz is
    signal s_cnt : integer range 0 to CNT_MAX := 0;
begin

    process(clk_i, rst_n_i, s_cnt)
    begin
        if(rst_n_i = '0')then --如果复位信号有效
            s_cnt <= 0;
            clk_o <= '0';
        elsif rising_edge(clk_i)then --如果在时钟信号上升沿
            if(s_cnt = CNT_MAX)then --计数到最大值
                s_cnt <= 0;
                clk_o <= '0';
            elsif(s_cnt = CNT_HALF)then --计数到一半
                s_cnt <= s_cnt + 1;
                clk_o <= '1';
            else
                s_cnt <= s_cnt + 1;
            end if;
        end if;
    end if;
end if;
```

```
end process;
```

```
end rtl;
```

数码管切换模块-shift，模块接收 400Hz 的信号，每一次上升沿时将输出的信号进行一次移位。

--模块名称: shift

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity shift is
```

```
    Port (
```

```
        clk_i : in  STD_LOGIC;    --时钟信号输入端
```

```
        rst_n_i : in  STD_LOGIC;  --复位信号输入端
```

```
        shift_o : out STD_LOGIC_VECTOR (7 downto 0) --输出端
```

```
    );
```

```
end shift;
```

```
architecture rtl of shift is
```

```
    signal s_shift : std_logic_vector(7 downto 0) := "01111111";
```

```
begin
```

```
    process(rst_n_i, clk_i, s_shift)
```

```
    begin
```

```
        if(rst_n_i = '0') then    --如果复位信号有效
```

```
            s_shift <= "01111111";
```

```
        elsif rising_edge(clk_i) then --如果在时钟信号上升沿
```

```
            s_shift <= s_shift(6 downto 0) & s_shift(7);
```

```
        end if;
```

```
    end process;
```

```
    shift_o <= s_shift;
```

```
end rtl;
```

译码器-decode，将接收端接收到的 BCD 数字翻译成数码管显示各数字所需要的编码，方便对数码管进行控制。

```
--模块名称: decode
```

```
--摘要提示:
```

```
--当前版本: 1.0.0
```

```
--模块作者:
```

```
--完成日期: 20xx 年 xx 月 xx 日
```

```
--内容提要:
```

```
--需要注意:
```

```
--取代版本:
```

```
--模块作者:
```

```
--完成日期:
```

```
--修改内容:
```

```
--修改文件:
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity decode is
```

```
    Port (
```

```
        seg7_BCDcode_i : in  STD_LOGIC_VECTOR (4 downto 0); --译码输入端
```

```
        seg7_decode_o : out STD_LOGIC_VECTOR (7 downto 0) --译码输出端
```

```
    );
```

```
end decode;
```

```
architecture rtl of decode is
```

```
begin
```

```
    process(seg7_BCDcode_i)
```

```
    begin
```

```
        case seg7_BCDcode_i is
```

```
            when "00000" => seg7_decode_o <= "11000000";
```

```
            when "00001" => seg7_decode_o <= "11111001";
```

```
            when "00010" => seg7_decode_o <= "10100100";
```

```
            when "00011" => seg7_decode_o <= "10110000";
```

```
            when "00100" => seg7_decode_o <= "10011001";
```

```
            when "00101" => seg7_decode_o <= "10010010";
```

```
            when "00110" => seg7_decode_o <= "10000010";
```

```
            when "00111" => seg7_decode_o <= "11111000";
```

```
            when "01000" => seg7_decode_o <= "10000000";
```

```

        when "01001" => seg7_decode_o <= "10010000";
        when others => seg7_decode_o <= "11000000";
    end case;
end process;
end rtl;

```

七段数码管显示模块-Seg7_disp, 该模块控制 8 个数码管中每个数码管的显示, 由 shift 模块发送来的信号控制所需要点亮的数码管, 即扫描, 切换频率为 400Hz。其中第三个和第六个数码管固定显示 “-”, 第一和第二个数码管显示时钟, 第四和第五个数码管显示分钟, 第七和第八个数码管显示秒钟, 显示的数字都是实时从各计时模块处理后发上来的数据

--模块名称: Seg7_disp

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

entity Seg7_disp is

```

```

    Port (

```

```

        shift_i :      in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_hour_h_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_hour_l_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_min_h_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_min_l_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_sec_h_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        disp_sec_l_i : in   STD_LOGIC_VECTOR(7 downto 0);

```

```

        seg7_code_o :      out  STD_LOGIC_VECTOR(7 downto 0)

```

```

    );

```

```

end Seg7_disp;

```

```

architecture rtl of Seg7_disp is

```

```

begin
  process(shift_i)
  begin
    case shift_i is
      when "11111110" => seg7_code_o <= disp_sec_l_i; --连接秒钟低位
      when "11111101" => seg7_code_o <= disp_sec_h_i; --连接秒钟高位
      when "11111011" => seg7_code_o <= "10111111";
      when "11110111" => seg7_code_o <= disp_min_l_i; --连接分钟低位
      when "11101111" => seg7_code_o <= disp_min_h_i; --连接分钟高位
      when "11011111" => seg7_code_o <= "10111111";
      when "10111111" => seg7_code_o <= disp_hour_l_i; --连接时钟低位
      when "01111111" => seg7_code_o <= disp_hour_h_i; --连接时钟高位
      when others      => seg7_code_o <= "10111111";
    end case;
  end process;
end rtl;

```

七段数码管总控制模块-Seg7_digital_LED,这一部分将 clk_gen_400hz 模块、shift 模块、decode 模块、Seg7_disp 模块集成在一起,封装成一个总的七段数码管控制模块,同时提供了时钟一些接口: 50mhz 信号接入口,复位信号接入口,时钟高位信号接入口,时钟低位信号接入口,分钟高位信号接入口,分钟低位信号接入口,秒钟高位信号接入口,秒钟低位信号接入口,数码管扫描控制端,七段数码管显示控制端。将数码管封装成这样的一个模块,使得对数码管的控制不需要考虑底层的内容,操控起来更加简单

--模块名称: Seg7_digital_LED

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

```

```

use IEEE.STD_LOGIC_ARITH.ALL;

```

```

use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity Seg7_digital_LED is

```



```

Port (
    clk_50mhz_i :    in    STD_LOGIC;
    rst_n_i :       in    STD_LOGIC;
    hour_h_i :       in    STD_LOGIC_VECTOR (4 downto 0);
    hour_l_i :       in    STD_LOGIC_VECTOR (4 downto 0);
    min_h_i :        in    STD_LOGIC_VECTOR (4 downto 0);
    min_l_i :        in    STD_LOGIC_VECTOR (4 downto 0);
    sec_h_i :        in    STD_LOGIC_VECTOR (4 downto 0);
    sec_l_i :        in    STD_LOGIC_VECTOR (4 downto 0);
    seg7_sel_o :     out    STD_LOGIC_VECTOR (7 downto 0);
    seg7_decode_o :  out    STD_LOGIC_VECTOR (7 downto 0)
);
end Seg7_digital_LED;

architecture rtl of Seg7_digital_LED is
    component clk_gen_400hz is
        port(
            rst_n_i : in    STD_LOGIC;
            clk_i :   in    STD_LOGIC;
            clk_o :   out   STD_LOGIC
        );
    end component;

    component shift is
        port(
            clk_i : in    STD_LOGIC;
            rst_n_i : in    STD_LOGIC;
            shift_o : out   STD_LOGIC_VECTOR (7 downto 0)
        );
    end component;

    component decode is
        port(
            seg7_BCDcode_i : in    STD_LOGIC_VECTOR (4 downto 0);
            seg7_decode_o : out    STD_LOGIC_VECTOR (7 downto 0)
        );
    end component;

    component Seg7_disp is
        port(
            shift_i :      in    STD_LOGIC_VECTOR(7 downto 0);
            disp_hour_h_i : in    STD_LOGIC_VECTOR(7 downto 0);
            disp_hour_l_i : in    STD_LOGIC_VECTOR(7 downto 0);
            disp_min_h_i :  in    STD_LOGIC_VECTOR(7 downto 0);

```

```

    disp_min_l_i : in STD_LOGIC_VECTOR(7 downto 0);
    disp_sec_h_i : in STD_LOGIC_VECTOR(7 downto 0);
    disp_sec_l_i : in STD_LOGIC_VECTOR(7 downto 0);
    seg7_code_o : out STD_LOGIC_VECTOR(7 downto 0)
);
end component;

signal s_400hz : std_logic;
signal s_shift : std_logic_vector(7 downto 0);
signal s_hour_h : std_logic_vector(7 downto 0);
signal s_hour_l : std_logic_vector(7 downto 0);
signal s_min_h : std_logic_vector(7 downto 0);
signal s_min_l : std_logic_vector(7 downto 0);
signal s_sec_h : std_logic_vector(7 downto 0);
signal s_sec_l : std_logic_vector(7 downto 0);

begin
    U1 : clk_gen_400hz port map(
        clk_i => clk_50mhz_i,
        rst_n_i => rst_n_i,
        clk_o => s_400hz
    );

    U2 : shift port map (
        clk_i => s_400hz,
        rst_n_i => rst_n_i,
        shift_o => s_shift
    );

    U3 : decode port map(
        seg7_BCDcode_i => hour_h_i,
        seg7_decode_o => s_hour_h
    );

    U4 : decode port map(
        seg7_BCDcode_i => hour_l_i,
        seg7_decode_o => s_hour_l
    );

    U5 : decode port map(
        seg7_BCDcode_i => min_h_i,
        seg7_decode_o => s_min_h
    );

    U6 : decode port map(
        seg7_BCDcode_i => min_l_i,

```

```

        seg7_decode_o => s_min_l
    );

U7 : decode port map(
    seg7_BCDcode_i => sec_h_i,
    seg7_decode_o => s_sec_h
);

U8 : decode port map(
    seg7_BCDcode_i => sec_l_i,
    seg7_decode_o => s_sec_l
);

U9 : Seg7_disp port map (
    shift_i => s_shift,
    disp_hour_h_i => s_hour_h,
    disp_hour_l_i => s_hour_l,
    disp_min_h_i => s_min_h,
    disp_min_l_i => s_min_l,
    disp_sec_h_i => s_sec_h,
    disp_sec_l_i => s_sec_l,
    seg7_code_o => seg7_decode_o
);

seg7_sel_o <= s_shift;
end rtl;

```

最后是 clock 模块，此模块综合了前面创建的所有的模块，形成一个电子钟。提供的接口为：50mHz 时钟信号接口，复位信号接口，七段数码管扫描端还有七段数码管显示端。50mHz 的时钟源分别在 clk_gen_1hz 和 clk_gen_400hz 模块中产生 1Hz 和 400Hz 的信号，1Hz 输入到 sec_counter 中产生秒数，进而控制 min_counter 和 hour_counter 产生分钟和时钟。三个计时器产生的数字都输出到 calc_mod 和 calc_rem 中提取出高位和低位，将结果输入到对应的 Seg7_digital_LED 模块的管脚，Seg7_digital_LED 模块会在其内部做各种处理，最后输出结果到七段数码管上。

--模块名称: clock

--摘要提示:

--当前版本: 1.0.0

--模块作者:

--完成日期: 20xx 年 xx 月 xx 日

--内容提要:

--需要注意:

--取代版本:

--模块作者:

--完成日期:

--修改内容:

--修改文件:

```
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity clock is
    Port (
        clk_50mhz_i : in  STD_LOGIC;    --系统时钟输入端
        rst_n_i      : in  STD_LOGIC;    --复位信号输入端
        seg7_sel_o   : out STD_LOGIC_VECTOR (7 downto 0); --七段数码管扫描
        seg7_code_o  : out STD_LOGIC_VECTOR (7 downto 0) --七段数码管显示
    );
end clock;

architecture rtl of clock is
    component clk_gen_1hz is
        port(
            rst_n_i : in  STD_LOGIC;
            clk_i   : in  STD_LOGIC;
            clk_o   : out STD_LOGIC
        );
    end component;

    component sec_counter is
        port(
            clk_i : in  STD_LOGIC;
            rst_n_i : in  STD_LOGIC;
            sec_cnt_o : out STD_LOGIC_VECTOR (5 downto 0);
            min_carry_o : out STD_LOGIC
        );
    end component;

    component min_counter is
        port(
            clk_i : in  STD_LOGIC;
            rst_n_i : in  STD_LOGIC;
            min_cnt_o : out STD_LOGIC_VECTOR (5 downto 0);
            hour_carry_o : out STD_LOGIC
        );
    end component;

    component hour_counter is
```

```

port(
    clk_i : in  STD_LOGIC;
    rst_n_i : in  STD_LOGIC;
    hour_cnt_o : out  STD_LOGIC_VECTOR (5 downto 0)
);
end component;

component calc_mod is
port(
    data_i : in  STD_LOGIC_VECTOR (5 downto 0);
    data_o : out  STD_LOGIC_VECTOR (4 downto 0)
);
end component;

component calc_rem is
port(
    data_i : in  STD_LOGIC_VECTOR (5 downto 0);
    data_o : out  STD_LOGIC_VECTOR (4 downto 0)
);
end component;

component Seg7_digital_LED is
port(
    clk_50mhz_i : in  STD_LOGIC;
    rst_n_i : in  STD_LOGIC;
    hour_h_i : in  STD_LOGIC_VECTOR (4 downto 0);
    hour_l_i : in  STD_LOGIC_VECTOR (4 downto 0);
    min_h_i : in  STD_LOGIC_VECTOR (4 downto 0);
    min_l_i : in  STD_LOGIC_VECTOR (4 downto 0);
    sec_h_i : in  STD_LOGIC_VECTOR (4 downto 0);
    sec_l_i : in  STD_LOGIC_VECTOR (4 downto 0);
    seg7_sel_o : out  STD_LOGIC_VECTOR (7 downto 0);
    seg7_decode_o : out  STD_LOGIC_VECTOR (7 downto 0)
);
end component;

signal s_1hz : std_logic;
signal s_1min : std_logic;
signal s_1hour : std_logic;
signal s_calc_sec : std_logic_vector(5 downto 0);
signal s_calc_min : std_logic_vector(5 downto 0);
signal s_calc_hour : std_logic_vector(5 downto 0);
signal s_sec_h : std_logic_vector(4 downto 0);
signal s_sec_l : std_logic_vector(4 downto 0);

```

```

signal s_min_h : std_logic_vector(4 downto 0);
signal s_min_l : std_logic_vector(4 downto 0);
signal s_hour_h : std_logic_vector(4 downto 0);
signal s_hour_l : std_logic_vector(4 downto 0);
begin
U1 : clk_gen_1hz port map(
    rst_n_i => rst_n_i,
    clk_i   => clk_50mhz_i,
    clk_o   => s_1hz
);
U2 : sec_counter port map(
    clk_i => s_1hz,
    rst_n_i => rst_n_i,
    sec_cnt_o => s_calc_sec,
    min_carry_o => s_1min
);
U3 : min_counter port map(
    clk_i => s_1min,
    rst_n_i => rst_n_i,
    min_cnt_o => s_calc_min,
    hour_carry_o => s_1hour
);
U4 : hour_counter port map(
    clk_i => s_1hour,
    rst_n_i => rst_n_i,
    hour_cnt_o => s_calc_hour
);

U5 : calc_mod port map (
    data_i => s_calc_sec,
    data_o => s_sec_h
);
U6 : calc_mod port map (
    data_i => s_calc_min,
    data_o => s_min_h
);
U7 : calc_mod port map (
    data_i => s_calc_hour,
    data_o => s_hour_h
);
U8 : calc_rem port map (
    data_i => s_calc_sec,
    data_o => s_sec_l
);

```

```

U9 : calc_rem port map (
    data_i => s_calc_min,
    data_o => s_min_l
);

U10 : calc_rem port map (
    data_i => s_calc_hour,
    data_o => s_hour_l
);

U11 : Seg7_digital_LED port map(
    clk_50mhz_i => clk_50mhz_i,
    rst_n_i => rst_n_i,
    hour_h_i => s_hour_h,
    hour_l_i => s_hour_l,
    min_h_i  => s_min_h,
    min_l_i  => s_min_l,
    sec_h_i  => s_sec_h,
    sec_l_i  => s_sec_l,
    seg7_sel_o => seg7_sel_o,
    seg7_decode_o => seg7_code_o
);

end rtl;

```

六、综合、仿真结果及分析：

1、RTL 级电路综合：

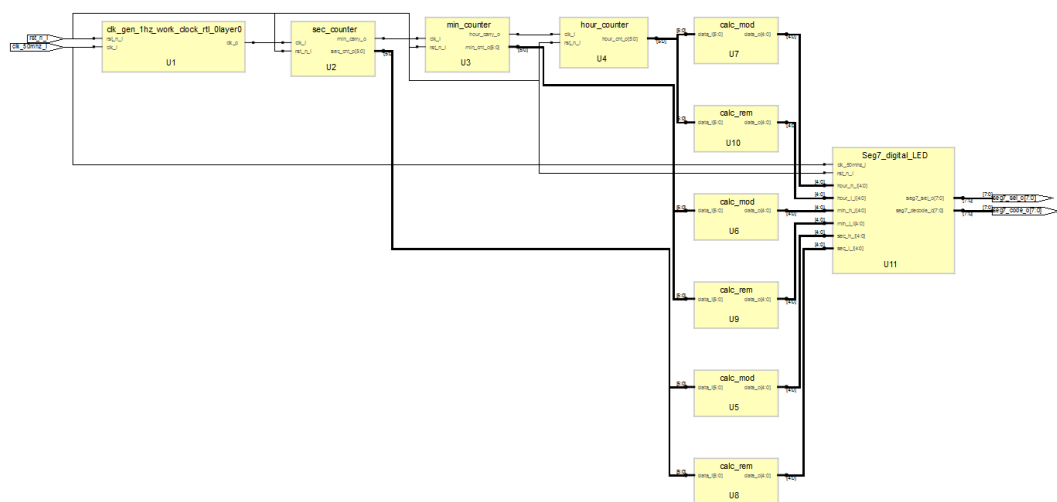


图 6-1

1Hz 时钟信号发生器电路图：

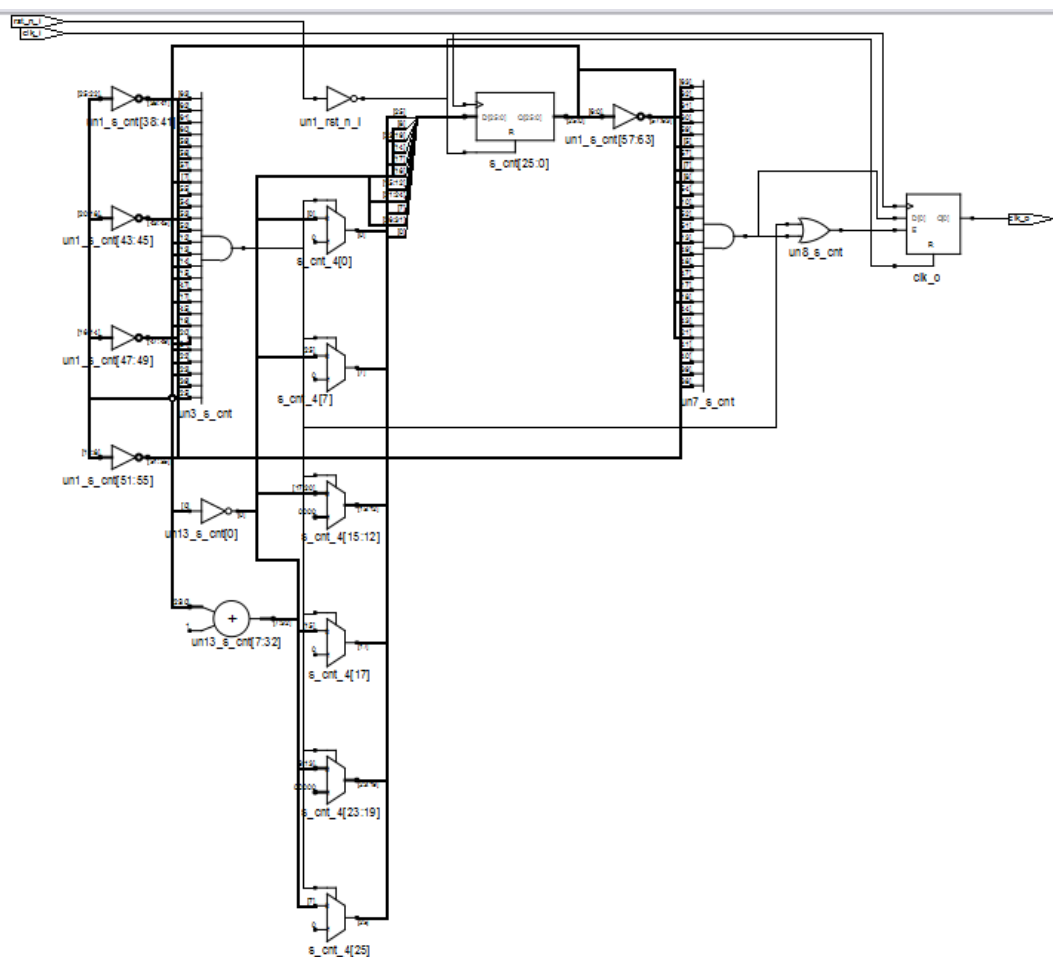


图 6-2

400Hz 时钟信号发生器电路图

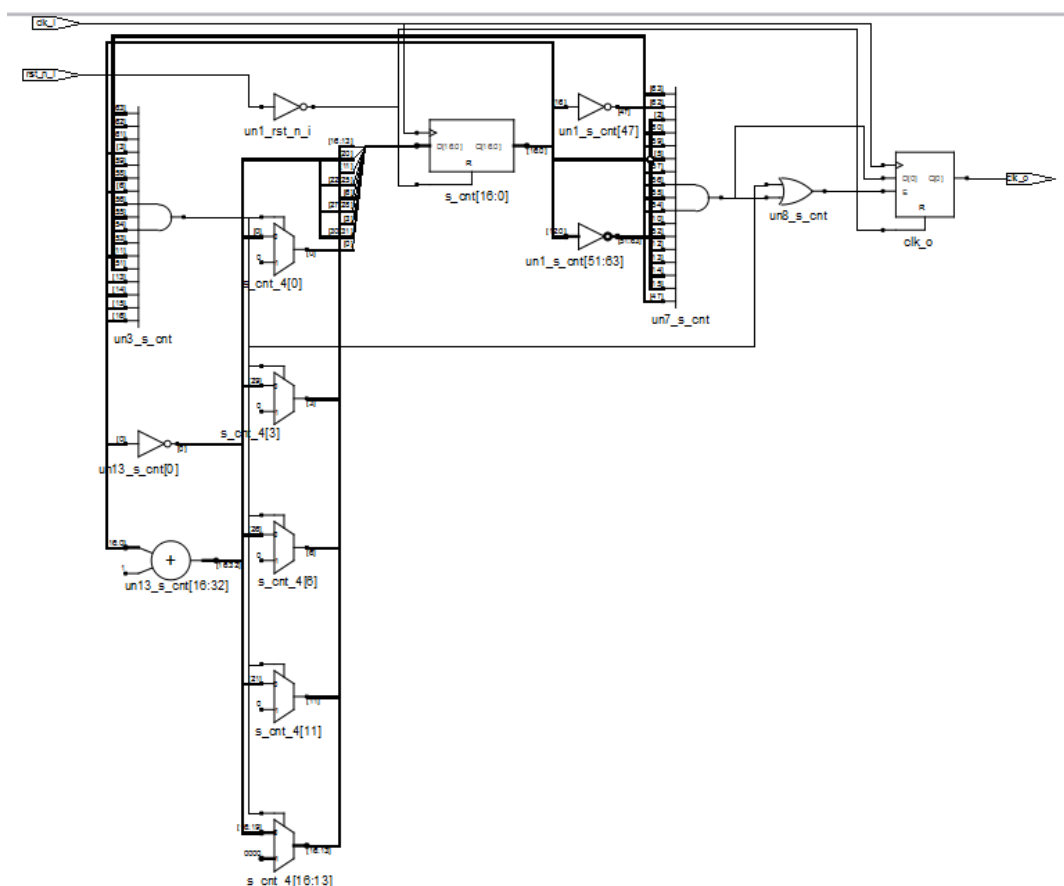


图 6-3

秒钟计数器电路图：

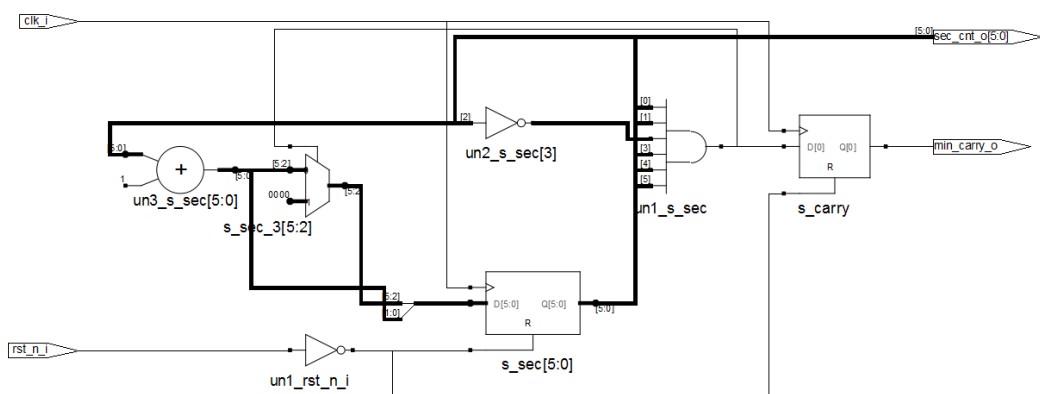


图 6-4

分钟计数器电路图

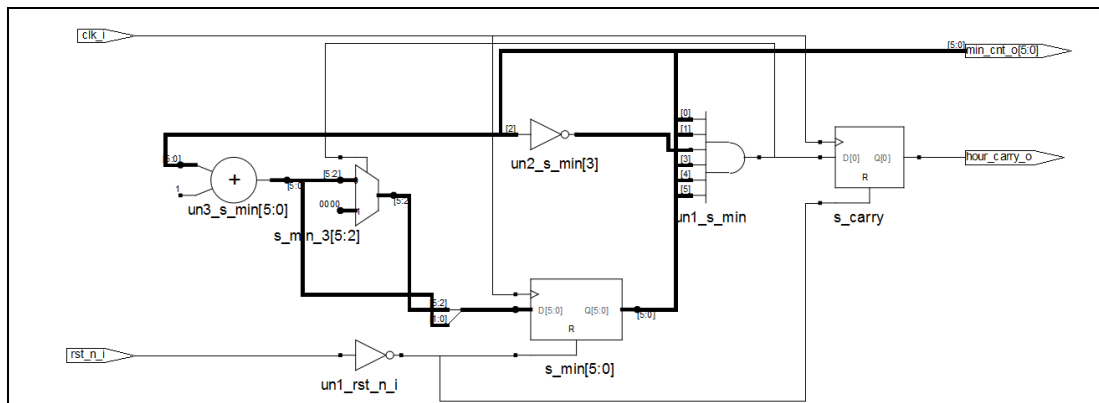


图 6-5

时钟计数器电路图


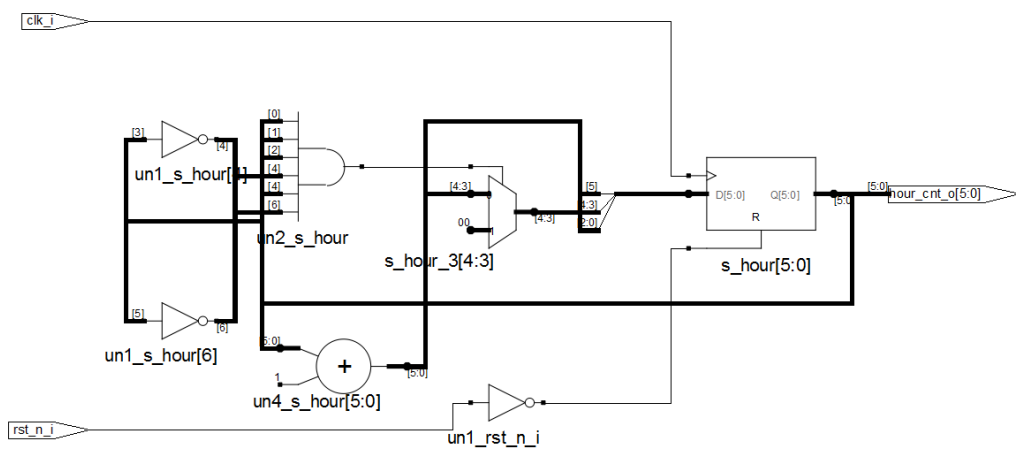


图 6-6

求商模块电路图

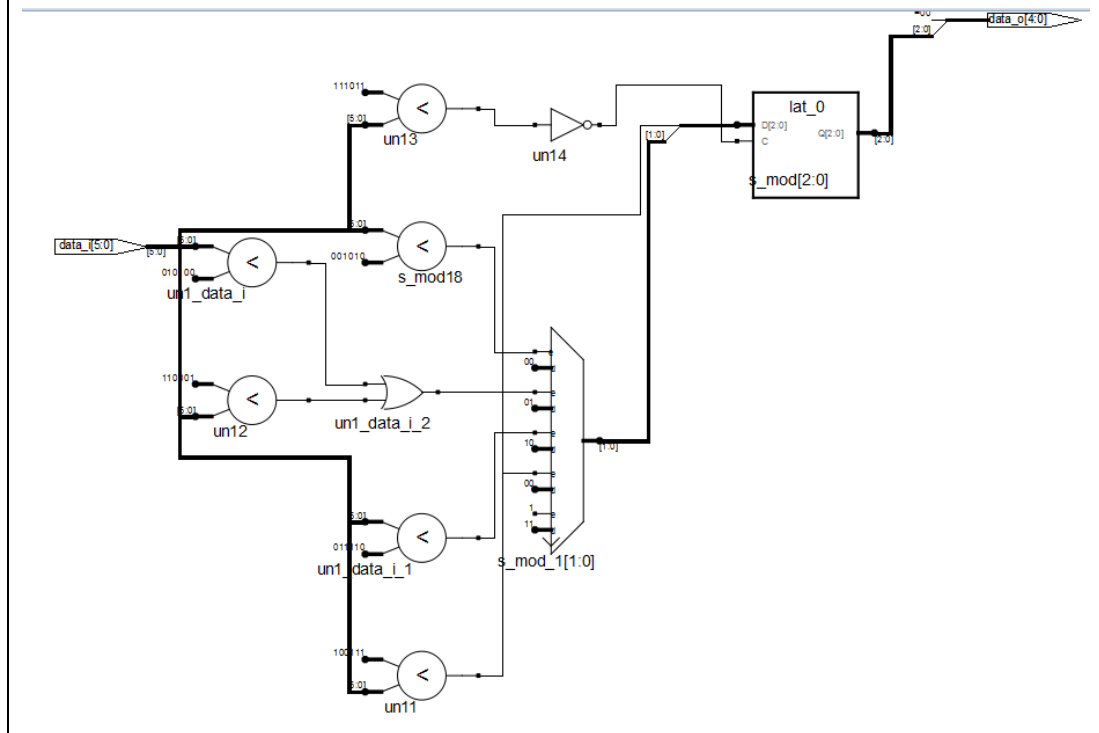

求模模块电路图

图 6-7

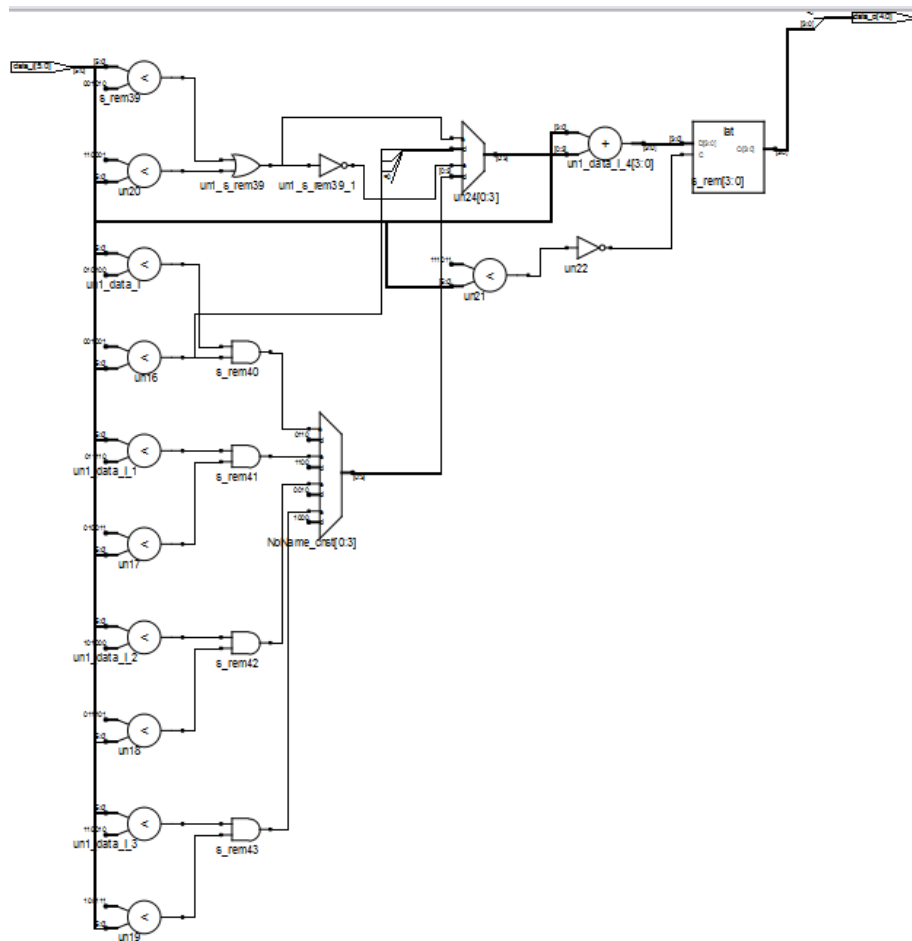


图 6-8

译码模块电路图

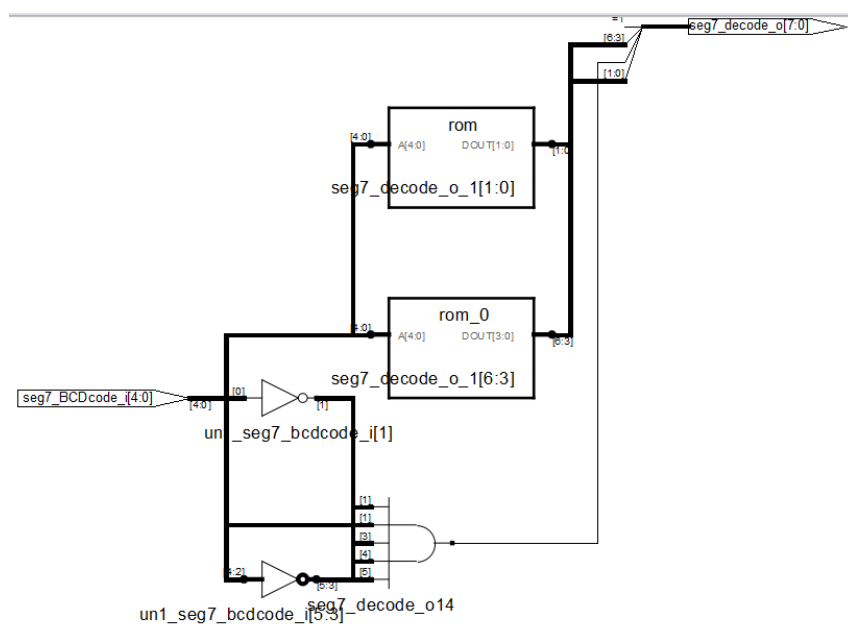


图 6-9

七段数码管显示模块电路图

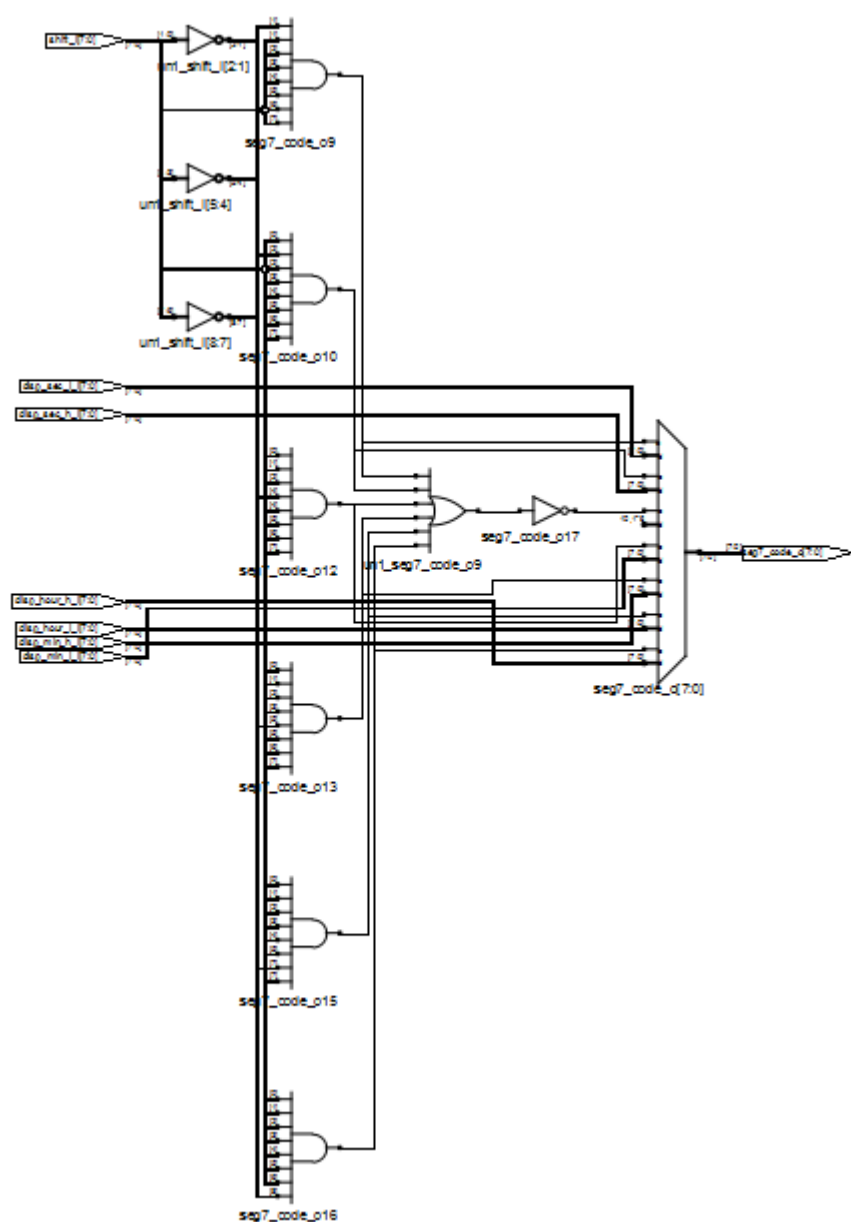


图 6-10

七段数码管总控制模块

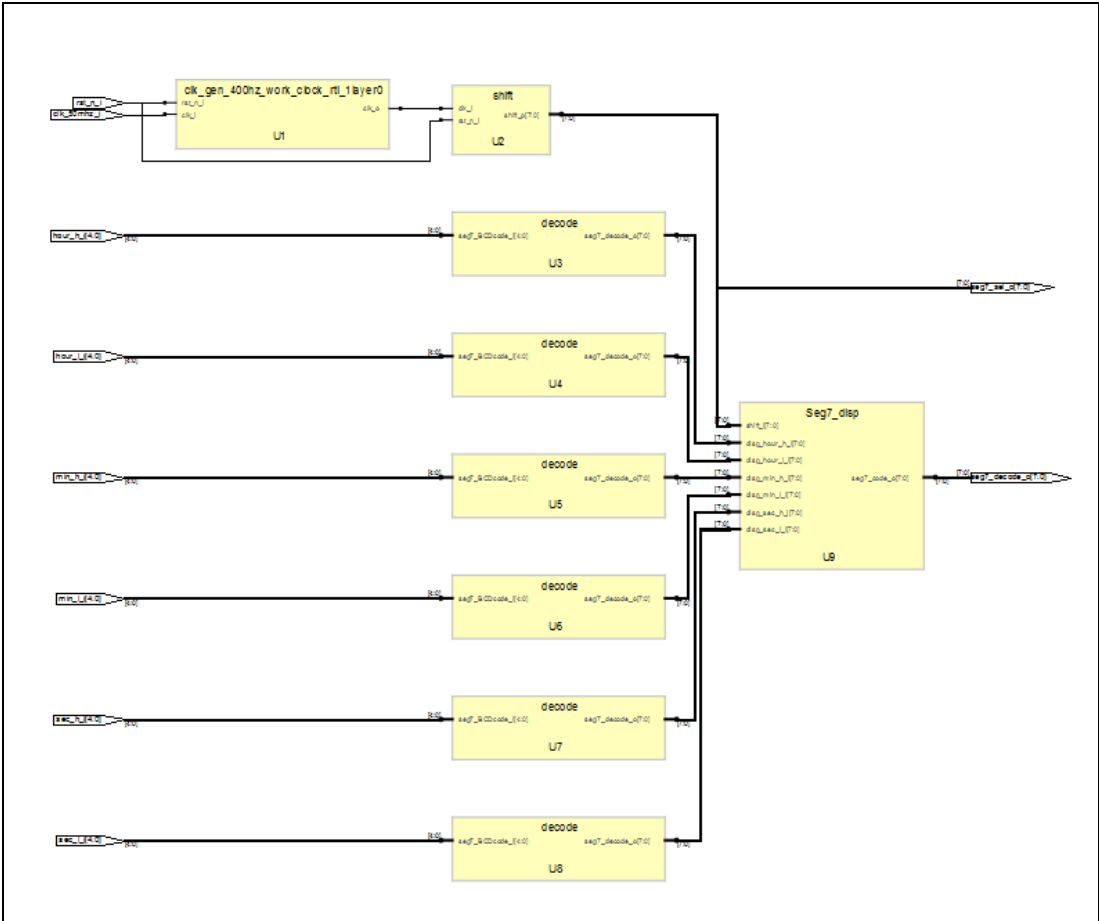


图 6-10

2、电路仿真

测试 sec_counter 和 decoder 的时序：
编写测试激励 Test Bench 代码如下：

--模块名称：decoder_tb
--摘要提示：译码器的测试激励文件
--当前版本：1.0.0
--模块作者：
--完成日期：20xx 年 xx 月 xx 日
--内容提要：
--需要注意：

--取代版本：
--模块作者：
--完成日期：
--修改内容：
--修改文件：

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```

ENTITY decode_tb IS
END decode_tb;

ARCHITECTURE behavior OF decode_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT decode
    PORT (
        seg7_BCDcode_i : IN  std_logic_vector(4 downto 0);
        seg7_decode_o  : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal seg7_BCDcode_i : std_logic_vector(4 downto 0) := (others =>
'0');

    --Outputs
    signal seg7_decode_o : std_logic_vector(7 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: decode PORT MAP (
        seg7_BCDcode_i => seg7_BCDcode_i,
        seg7_decode_o => seg7_decode_o
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        seg7_BCDcode_i <= "10001";

        -- insert stimulus here

        wait;
    end process;

```

END;

仿真得到的结果如图 6-11 所示

 


图 6-11

输入 10001（9），输出的结果是 11000000，数码管显示 9，说明模块设计是正确的

--模块名称: sec_counter
--摘要提示: 秒钟计数器的测试激励文件
--当前版本: 1.0.0
--模块作者:
--完成日期: 20xx 年 xx 月 xx 日
--内容提要:
--需要注意:

--取代版本:
--模块作者:
--完成日期:
--修改内容:
--修改文件:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY sec_counter_tb IS
END sec_counter_tb;

ARCHITECTURE behavior OF sec_counter_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT sec_counter
    PORT (
        clk_i : IN std_logic;
        rst_n_i : IN std_logic;
        sec_cnt_o : OUT std_logic_vector(5 downto 0);
        min_carry_o : OUT std_logic
    );
    END COMPONENT;
```

```

--Inputs
signal clk_i : std_logic := '0';
signal rst_n_i : std_logic := '0';

--Outputs
signal sec_cnt_o : std_logic_vector(5 downto 0);
signal min_carry_o : std_logic;

-- Clock period definitions
constant clk_i_period : time := 20 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: sec_counter PORT MAP (
    clk_i => clk_i,
    rst_n_i => rst_n_i,
    sec_cnt_o => sec_cnt_o,
    min_carry_o => min_carry_o
  );

-- Clock process definitions
clk_i_process :process
begin
  clk_i <= '0';
  wait for clk_i_period/2;
  clk_i <= '1';
  wait for clk_i_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
  -- hold reset state for 100 ns.
  wait for 100 ns;

  wait for clk_i_period*10;

  -- insert stimulus here
  rst_n_i <= '1';

  wait;
end process;

```


END;

仿真结果如图 6-12 所示：

 


图 6-12

每 60s 会输出一个分钟进位，每个时钟上升沿都会改变 sec_cnt_o 的输出（图片被缩略未显示），证明模块设计是正确的。

七、FPGA 板级验证及结果分析

1、在工程中加入引脚约束文件 clock.ucf，代码如下

```
Net "clk_50mhz_i"      LOC=P129;
Net "rst_n_i"          LOC=P85;

Net "seg7_sel_o<7>" LOC=P8;
Net "seg7_sel_o<6>" LOC=P14;
Net "seg7_sel_o<5>" LOC=P15;
Net "seg7_sel_o<4>" LOC=P16;
Net "seg7_sel_o<3>" LOC=P17;
Net "seg7_sel_o<2>" LOC=P20;
Net "seg7_sel_o<1>" LOC=P21;
Net "seg7_sel_o<0>" LOC=P22;

Net "seg7_code_o<7>" LOC=P139;
Net "seg7_code_o<6>" LOC=P140;
Net "seg7_code_o<5>" LOC=P142;
Net "seg7_code_o<4>" LOC=P2;
Net "seg7_code_o<3>" LOC=P3;
Net "seg7_code_o<2>" LOC=P4;
Net "seg7_code_o<1>" LOC=P5;
Net "seg7_code_o<0>" LOC=P7;
```

综合之后生成 bit 文件烧进实验箱中观察到如下图 7-1 和图 7-2 的现象：



图 7-1



图 7-2

经过验证，电子钟可以正确显示时间，而且各级的进位也没有问题。

实验总结:

通过这次实验的学习,我学会了利用 FPGA 芯片的模块化的方法实现系统,懂得了将大的问题细分成一个个小的模块,逐个实现它们,最后在组装在一起,来实现我们所需要的功能。掌握了分频的方法。成功编写出了电子钟模块,能够将各种模块例化并使用它们,即顶层模块调用底层模块,而且学会了嵌套调用模块。

指导教师批阅意见：

成绩评定：

指导教师签字：

年 月 日

备注：

注：1、报告内的项目或内容设置，可根据实际情况加以调整和补充。

2、教师批改学生实验报告时间应在学生提交实验报告时间后 10 日内。